

Continue



The disadvantage of the one wattmeter method is that it cannot be used for three-phase systems that carry unbalanced loads. Also, in three wattmeter method for star-connected load, it is difficult to get a neutral point to connect voltage coils, and the current coils are inserted in a closed delta for delta connected load. These drawbacks can be overcome by the Two Wattmeter method. The two wattmeter method of three-phase power measurement is given from Blondel's theorem. Blondel's Theorem for 3-Phase Power Measurement : Blondel's theorem tells about the number of wattmeters required to measure three-phase power. It states that, in order to measure power in a network with n number of lines. The total number of wattmeters required is equal to n, and total power is the sum of all the wattmeters readings. It is in such condition that, if current coils of each wattmeter are connected in each line and corresponding voltage coils are connected such that, one end to their respective line and other ends of all the voltage coils are connected together forming a common point. Suppose, if the common point is to be taken on any one of the lines. Then the other end of the voltage coils is connected to that common line (i.e., common point). In such conditions, the power can be measured by (n-1) wattmeters. Thus for measuring 3-phase power, only 2 wattmeters are required, this is called Two Wattmeter Method. Measurement of Power by Two Wattmeter Method : This method is employed for the power measurement of a 3-phase 3-wire unbalanced or balanced system. The current coils are connected in series with the two lines. One end of each voltage coil is connected to the line in which current coils are placed and the other ends of two voltage coils are brought out and are connected to the third line. The connection diagram for the two wattmeter method of measuring the three-phase power of star and delta connected loads is shown below. Measurement of Power by Two Wattmeter Method in Star Connection : Let the phase voltages and line currents of the phases R, Y, and B be (VR & IR), (VY & IY), and (VB & IB). Let W1 and W2 be the power measured by wattmeters 1 and 2 respectively. From the above figure, the power measurement by wattmeter 1 is, W1 = (VR - VY) IR = VR IR - VY IR Power measurement by wattmeter 2 is, W2 = (VB - VY) IB = VB IB - VY IB At neutral point N, we have, Therefore, total power i.e., sum of both the wattmeter readings is, Hence, the sum of both the wattmeter readings gives the total power consumed by the load. Measurement of Power by Two Wattmeter Method in Delta Connection : Let the phase voltages and line currents of the phases R, Y, and B be (VR & IR), (VY & IY), and (VB & IB). Let W1 and W2 be the power measured by wattmeters 1 and 2 respectively. From the above figure, the power measurement by wattmeter 1 is, W1 = (VR - IR) IB = VR IR - IR IB Power measurement by wattmeter 2 is, W2 = -VY (IB - IY) = VY IB - VY IY Here, VY is taken as negative because it is being measured from phase B to Y while VY is from Y to B. Applying KVL to the delta connected load, we get, Therefore, total power i.e., sum of both the wattmeter readings is, In this case also, the sum of both the wattmeter readings gives the total power consumed by the load. Hence, at any instant regardless of the power factor, the sum of two wattmeter readings gives total instantaneous power in a three-phase unbalanced load. Sign Up Now & Daily Live Classes3000+ TestsStudy Material & PDFQuizzes With Detailed Analytics+ More BenefitsGet Free Access Now Two Wattmeter Method of power measurement can be used for both the balanced or unbalanced loads of 3 Φ 4 wires or 3 Φ 3 wire systems. In this method two wattmeters are connected as shown in Fig. 1. The current coils are connected in series with the load and the pressure coils are connected across the line voltage. The total power consumed by the load is the algebraic sum of both wattmeters reading keeping in view the value of power factor of the load i.e. p = W1 + W2 In this method, the current coil of the two wattmeters are connected in any of the two lines and the potential coil of both wattmeters are connected with the left third line, in which no wattmeter is connected. Star Connected Load The Fig. 1. shows arrangement of wattmeter for a 3-phase star connected load. Fig. 1. Two Wattmeter Method for Star Connected Load. Let v1, v2, v3 are the instantaneous voltages and i1, i2, and i3 are the instantaneous value of currents. As, these are the instantaneous values therefore, instantaneous power will be equal to the sum of their products i.e., instantaneous power p = v1 i1 + v2 i2 + v3 i3 . . . (i) It can be proved, that the total power will be the algebraic sum of the readings of the two wattmeters. If readings of the wattmeters are W1 and W2, the total power = W1 + W2. Proof: Since all the three phases meet at a star point, according to the Kirchhoff's currents law (KCL), the algebraic sum of the currents will be zero, i.e., i1 + i2 + i3 = 0 or i3 = -(i1 + i2) . . . (ii) Substituting this value in expression (i). The instantaneous total power will be p = v1 i1 + v2 i2 + v3 (i1 + i2) = v1 i1 + v2 i2 - v3 i1 - v3 i2 p = i1 (v1 - v3) + i2 (v2 - v3) . . . (iii) As i1 is the instantaneous current flowing through the current coil of wattmeter w1 and (v1 - v3) is the potential difference acting across its potential coil hence, i1 (v1 - v3) = W1 Similarly, i2 is the instantaneous current flowing through the current coil of wattmeter W2 and (v2 - v3) is the potential difference acting across its potential coil hence, i2 (v2 - v3) = W2 Hence, total instantaneous power, p = W1 + W2 Delta Connected Load The Fig. 2 shows wattmeters connections for 3-phase delta connected load. Fig. 2. Two Wattmeter Method for Delta Connected Load In delta, as the three phases form a closed loop and according to the Kirchhoff voltage law (KVL) v1 + v2 + v3 = 0 or v1 = -(v2 + v3) The instantaneous total power will be p = v1 i1 + v2 i2 + v3 i3 . . . (iv) Substituting in eq. (iv) v1 = -(v2 + v3) we get p = -(v2 + v3) i1 + v2 i2 + v3 i3 p = -v3 (i1 - i3) + v1 (i2 - i1) . . . (v) As -v3 is the instantaneous potential difference across potential coil of wattmeter W2 and (i1 - i3) is the instantaneous current flowing through its current coil hence, v1 (i2 - i1) = W2 Hence, total instantaneous power (From eq. (v)) p = W1 + W2 Result: Hence, the algebraic sum of two wattmeters' readings give the total power of the circuit irrespective that it is star or delta connected or it is balanced or unbalanced. Depending upon the power factor, the readings of the wattmeters are affected. There are the following different cases. (i) When power factor is unity. In this case both the wattmeters will give positive readings and equal also. (ii) When Power factor ≥ 0.5. Both wattmeters will read positive but different readings. In case if the power factor is 0.5, only one wattmeter will give reading and total power will be equal to this reading. (iii) When power factor < 0.5. In this case the one wattmeter will read in opposite direction, change the connection of the current coil of this wattmeter and get positive reading. This article explains the measurement of three-phase power in star connected or delta connected load using the wattmeter methods. The power in a three phase load can be measured by following methods: Three wattmeter method Two wattmeter method One wattmeter method The name of these methods indicates the number of wattmeters used in the measurement of the three-phase power. What is a Wattmeter? A wattmeter is an equipment used to measure power in a circuit. It consists of two types of coils. They are: A Current Coil that possesses a low resistance. A Pressure or Potential Coil that possesses a high resistance. The current coil is connected in series with the line carrying current. The pressure coil is connected across the two points whose potential difference is to be measured. Refer the figure for the connections of a wattmeter. Connection of a Wattmeter A wattmeter shows a reading which proportional to the product of three values. They are: Current (I) through its current coil. Potential difference (V) across its pressure coil. Cosine of the angle between voltage and current (Cosφ). P = VI Cos(φ) A comparison between the methods of measuring power in a three-phase circuit is shown in the table below. Three Wattmeter Method Used for measurement of 3 phase, 4 wire circuits. Both balanced and unbalanced loads. One Wattmeter Method Used in Balanced 3 phase, 3 wire load circuit. Two Wattmeter Method Used in both balanced and unbalanced 3 phase, 3 wire circuits. Now we will explain the measurement three-phase power measurement using three wattmeter method. Three wattmeter method is used to measure power in 3 phase, 4-wire circuits. However, this method can also be used in 3 phase, 3 wire delta connected load, where power consumed by each load is required to be determined separately. The figure below shows the three wattmeter connection of 3 phase, 4 wire star connected load. Three Wattmeter Methods indicated in the figure, the three wattmeters are connected in each of the three phases to measure three-phase power usage of the load whether star or delta connected. The current coil of each wattmeter carries the current of one phase only and the pressure coil measures the phase voltage of the phase. Hence, each wattmeter measures the power in a single phase. The total power in the load is given by the algebraic sum of the readings of the three wattmeters. P = W1 + W2 + W3 where, W1 = V1 I1, W2 = V2 I2, W3 = V3 I3 While using three wattmeter method following difficulty is met with: In the case of 3 phase, 3 wire star connected load, it is difficult to get a neutral point which is required for connection. In special cases, when this method is necessary to use, an 'artificial star' can be formed. In case of delta connected circuits, the difficulty in using this method is due to fact that the phase coils are required to be broken for inserting current coils of wattmeters. To measure power it is not necessary to use three wattmeter, even two wattmeters can be used for the purpose. Except for 3 phase, 4 wire unbalanced load, three-phase power are measured using only Two Wattmeter Method. The next method we are going to discuss is the one wattmeter method. In this method of three-phase power measurement, the current coil is connected in any one line and the pressure coil is connected alternatively between this and the other two lines. The connection diagram is shown in the figure below. One Wattmeter Method So we will get two readings for a balanced load. The two readings so obtained, correspond to those obtained by the normal two wattmeter method. A balanced load is a load that draws the same current from each phase of the three-phase system, while an unbalanced load has at least one of those currents different from the rest. In balanced 3-wire, 3-phase load circuit the power in each phase is equal. Therefore, the total power of the circuit can be determined by multiplying the power measured in any one phase by three. Total power in balanced load = 3 x Power per Phase = 3 x Wattmeter reading This method is not of as much universal application as the two wattmeter method because it is restricted to fairly balanced loads only. Even a slight degree of unbalance in the loading produce a large error in the measurement. However, it may be conveniently applied, for instance, when it is desired to find the power input to a factory motor in order to check the load up on the motor. As the name indicates, in this method two wattmeters are used to measure three-phase power. This is the most popular method among the three. This method is generally used for the measurement of power in 3 phase, 3-wire load circuits. It can be used to measure power in star/delta connected load in balanced or unbalanced condition. Remember a balanced load is a load that draws the same current from each phase of the three-phase system, while an unbalanced load has at least one of those currents different from the rest. In two wattmeter method, the current coils of the two wattmeters are inserted in any two lines and pressure coil of each wattmeter is joined to the third line. Refer the figure below for better understanding. Two Wattmeter Method The figure above shows the two wattmeter connection of star connected load. Similarly, delta connected loads are also used. Two wattmeter method can be used irrespective of balanced or unbalanced load. The algebraic sum of two wattmeter reading gives the total power in the 3-phase, 3 wire star-connected or delta connected load circuits whether the load is balanced or unbalanced. P = W1 + W2 WORKED EXAMPLES THREE PHASE POWER MEASUREMENT By 2 wattmeter method Case (a): Balanced star connected loads. COM Example 13 Determine the power and power factor of the two wattmeters read (i) 1000 W each, both positive (ii) 1000 W each of opposite sign. Solution: Case (i): W1 = 1000 watts W2 = 1000 watts This power factor may be lead or lag. As the load is not specified, (inductive or capacitive) we can not identify the nature of power factor. Example 14 The power input to a 2000 V, 50 Hz, 36 motor running on full load at an efficiency of 90% is measured by two wattmeters which indicate 300KW and 100KW respectively. Calculate i) Input, ii) Power factor, iii) Line current, iv) H.P. output. Solution: W1 = 300 KW W2 = 100 KW i) Total input power = W1 + W2 = 400 KW = 400 × 103 W ii) The motor is assumed to be induction motor. Hence the power factor is lagging in nature. Example 15 In a balanced 34 system, the power is measured by two-wattmeter method and the ratio of two wattmeter readings is 2: 1. Determine the power factor of the system. Solution: Data: W2 / W1 = 1/2 = p (say) We know that for lagging power factor, Example 16 A balanced delta connected load takes a line current of 15A when connected to a 400 V system. A wattmeter with its current coil in one line and potential coil between the two remaining lines read 2000 W. Describe the load impedance. Solution : For this type of connection, the wattmeter indicates reactive power. Hence the given power must be in VAR and not watts. Watt meter reading Example 17 Three identical coils each having a resistance of 202 and a reactance of 202 are connected in i) star ii) delta across 440 V, 3 phase supply. Calculate for each case, line current and reading in each of the wattmeters connected to measure power. Solution: All the electrical equipment and machines work on supplying electric power and dissipate large amounts of energy. The supplied power is usually measured in terms of watts using a device namely wattmeter. A wattmeter is also called as deflection meter which is mainly used in electrical labs. It not only measure power in terms of watts but also measures in terms of kilowatts and megawatts. The wattmeter usually consists of two coils "CC" current coil which is usually connected in series with load current and a voltage/pressure /potential coil "PC", this coil is usually connected across the load circuit. The electrical power can be represented in three forms they are real power, reactive power, and apparent power. The following article describes the two wattmeter method at balanced load condition. What is Two Wattmeter Method? A three-phase two-watt meter measures the current and voltage from any of the 2 supply lines of 3 phase corresponding to the 3rd supply line of 3 phase. The 3 phase 2 wattmeter is said to be at a balanced load condition if the current in every phase lag at an angle "φ" with phase voltage. Construction of Two Wattmeter Method The 3-phase power of a 3-phase circuit can be measured using 3 ways they are, 3 Wattmeter Method 2 Wattmeter Method 1 Wattmeter Method. The main concept of 2 Wattmeter with 3 phase voltage is to balance the 3 phase load by satisfying the condition of current lagging at an angle "φ" with the voltage phase. The schematic diagram of 3 phase 2 wattmeter is shown below Circuit Diagram It consists of 2 wattmeters like W1 and W2, where each wattmeter has a current coil 'CC' and a pressure coil 'PC'. Here, one end of wattmeter 'W1' is connected to 'R' terminal whereas one end of wattmeter 'W2' is connected to 'Y' terminal. The circuit also consists of 3 inductors 'Z' which are constructed in a star topology. The 2 ends of inductors are connected to 2 terminals of a wattmeter whereas the third terminal of the inductor is connected to B. Derivation of Two Wattmeter Method Two Wattmeter is used to determine two main parameters they are, Power factor Reactive power. Consider the load used as an inductive load which is represented by following the phasor diagram as shown below. Phasor Diagram The voltages VRN, VYN, and VBN are electrically 1200 in phase with one other, we can observe that the current phase lags at the "φ" angle with voltage phase. The current in wattmeter W1 is represented as W1 = IR (1) where IR is current The potential difference across the wattmeter W1 coil is given as W1 = - VRB = | - VRN - VBN | (2) Where VRN and VBN are voltages The phase difference between the voltage 'YB' and current 'IY' is given as (300 + φ) Hence the power measured by wattmeter is given as W2 = YB IY cos (300 + φ) (3) At balanced load condition, IR = IY = IB = IL and (4) VRY = YB = VBR = VL (5) Therefore we obtain wattmeter readings as W1 = VL IL cos (300 - φ) and (6) W2 = VL IL cos (300 + φ) (7) Total Power Derivation The total wattmeter reading is given as W1 + W2 = VL IL cos (300 - φ) + VL IL cos (300 + φ) (8) = VL IL [cos (300 - φ) + cos (300 + φ)] = VL IL [cos 300 cos φ + sin 300 sin φ + cos 300 cos φ - sin 300 sin φ] = VL IL [2 cos 300 cos φ] = VL IL [(2 √3 / 2) cos 300 cos φ] = √3 [VL IL cos φ] (9) W1 + W2 = P (10) Where 'P' is the total observed power in a 3-phase balanced load condition. Power Factor Derivation Definition: It is the ratio between actual power observed by the load to apparent power flowing in the circuit. The power factor of three phase balanced load condition can be determined and derived from wattmeter readings as follows From equation 9 W1 + W2 = √3 VL IL cos φ Now W1 - W2 = VL IL [cos (300 - φ) - cos (300 + φ)] = VL IL [cos 300 cos φ + sin 300 sin φ - cos 300 cos φ + sin 300 sin φ] = 2 VL IL sin 300 sin φ W1 - W2 = VL IL sin φ (11) Dividing equations 11 and 9 (W1 - W2) / (W1 + W2) = VL IL sin φ / √3 VL IL cos φ Tan φ = √3 (W1 - W2) / (W1 + W2) The power factor of the load is given as cos φ = cos tan-1 [√3 (W1 - W2) / (W1 + W2)] (12) Reactive Power Derivation Definition: It is the ratio between complex power corresponding to storage and revival of energy rather than consumption. To obtain reactive power, we multiply equation 11 with √3 (W1 - W2) = √3 [VL IL sin φ] = Pr = √3 (W1 - W2) (13) Where Pr is the reactive power obtained from 2 wattmeters. Two Wattmeter Method Table The two wattmeter method observations can be noted practically by following the table. S.NO Voltage VL (volts) Current IL (amp) Power W1 (watts) Power W2 (watts) Total Power P = W1 + W2 Power Factor = cos φ 1 2 3 4 5 6 7 8 9 10 11 12 13 14 15 16 17 18 19 20 21 22 23 24 25 26 27 28 29 30 31 32 33 34 35 36 37 38 39 40 41 42 43 44 45 46 47 48 49 50 51 52 53 54 55 56 57 58 59 60 61 62 63 64 65 66 67 68 69 70 71 72 73 74 75 76 77 78 79 80 81 82 83 84 85 86 87 88 89 90 91 92 93 94 95 96 97 98 99 100 101 102 103 104 105 106 107 108 109 110 111 112 113 114 115 116 117 118 119 120 121 122 123 124 125 126 127 128 129 130 131 132 133 134 135 136 137 138 139 140 141 142 143 144 145 146 147 148 149 150 151 152 153 154 155 156 157 158 159 160 161 162 163 164 165 166 167 168 169 170 171 172 173 174 175 176 177 178 179 180 181 182 183 184 185 186 187 188 189 190 191 192 193 194 195 196 197 198 199 200 201 202 203 204 205 206 207 208 209 210 211 212 213 214 215 216 217 218 219 220 221 222 223 224 225 226 227 228 229 230 231 232 233 234 235 236 237 238 239 240 241 242 243 244 245 246 247 248 249 250 251 252 253 254 255 256 257 258 259 260 261 262 263 264 265 266 267 268 269 270 271 272 273 274 275 276 277 278 279 280 281 282 283 284 285 286 287 288 289 290 291 292 293 294 295 296 297 298 299 300 301 302 303 304 305 306 307 308 309 310 311 312 313 314 315 316 317 318 319 320 321 322 323 324 325 326 327 328 329 330 331 332 333 334 335 336 337 338 339 340 341 342 343 344 345 346 347 348 349 350 351 352 353 354 355 356 357 358 359 360 361 362 363 364 365 366 367 368 369 370 371 372 373 374 375 376 377 378 379 380 381 382 383 384 385 386 387 388 389 390 391 392 393 394 395 396 397 398 399 400 401 402 403 404 405 406 407 408 409 410 411 412 413 414 415 416 417 418 419 420 421 422 423 424 425 426 427 428 429 430 431 432 433 434 435 436 437 438 439 440 441 442 443 444 445 446 447 448 449 450 451 452 453 454 455 456 457 458 459 460 461 462 463 464 465 466 467 468 469 470 471 472 473 474 475 476 477 478 479 480 481 482 483 484 485 486 487 488 489 490 491 492 493 494 495 496 497 498 499 500 501 502 503 504 505 506 507 508 509 510 511 512 513 514 515 516 517 518 519 520 521 522 523 524 525 526 527 528 529 530 531 532 533 534 535 536 537 538 539 540 541 542 543 544 545 546 547 548 549 550 551 552 553 554 555 556 557 558 559 560 561 562 563 564 565 566 567 568 569 570 571 572 573 574 575 576 577 578 579 580 581 582 583 584 585 586 587 588 589 590 591 592 593 594 595 596 597 598 599 600 601 602 603 604 605 606 607 608 609 610 611 612 613 614 615 616 617 618 619 620 621 622 623 624 625 626 627 628 629 630 631 632 633 634 635 636 637 638 639 640 641 642 643 644 645 646 647 648 649 650 651 652 653 654 655 656 657 658 659 660 661 662 663 664 665 666 667 668 669 670 671 672 673 674 675 676 677 678 679 680 681 682 683 684 685 686 687 688 689 690 691 692 693 694 695 696 697 698 699 700 701 702 703 704 705 706 707 708 709 710 711 712 713 714 715 716 717 718 719 720 721 722 723 724 725 726 727 728 729 730 731 732 733 734 735 736 737 738 739 740 741 742 743 744 745 746 747 748 749 750 751 752 753 754 755 756 757 758 759 760 761 762 763 764 765 766 767 768 769 770 771 772 773 774 775 776 777 778 779 780 781 782 783 784 785 786 787 788 789 790 791 792 793 794 795 796 797 798 799 800 801 802 803 804 805 806 807 808 809 810 811 812 813 814 815 816 817 818 819 820 821 822 823 824 825 826 827 828 829 830 831 832 833 834 835 836 837 838 839 840 841 842 843 844 845 846 847 848 849 850 851 852 853 854 855 856 857 858 859 860 861 862 863 864 865 866 867 868 869 870 871 872 873 874 875 876 877 878 879 880 881 882 883 884 885 886 887 888 889 890 891 892 893 894 895 896 897 898 899 900 901 902 903 904 905 906 907 908 909 910 911 912 913 914 915 916 917 918 919 920 921 922 923 924 925 926 927 928 929 930 931 932 933 934 935 936 937 938 939 940 941 942 943 944 945 946 947 948 949 950 951 952 953 954 955 956 957 958 959 960 961 962 963 964 965 966 967 968 969 970 971 972 973 974 975 976 977 978 979 980 981 982 983 984 985 986 987 988 989 990 991 992 993 994 995 996 997 998 999 1000 1001 1002 1003 1004 1005 1006 1007 1008 1009 1010 1011 1012 1013 1014 1015 1016 1017 1018 1019 1020 1021 1022 1023 1024 1025 1026 1027 1028 1029 1030 1031 1032 1033 1034 1035 1036 1037 1038 1039 1040 1041 1042 1043 1044 1045 1046 1047 1048 1049 1050 1051 1052 1053 1054 1055 1056 1057 1058 1059 1060 1061 1062 1063 1064 1065 1066 1067 1068 1069 1070 1071 1072 1073 1074 1075 1076 1077 1078 1079 1080 1081 1082 1083 1084 1085 1086 1087 1088 1089 1090 1091 1092 1093 1094 1095 1096 1097 1098 1099 1100 1101 1102 1103 1104 1105 1106 1107 1108 1109 1110 1111 1112 1113 1114 1115 1116 1117 1118 1119 1120 1121 1122 1123 1124 1125 1126 1127 1128 1129 1130 1131 1132 1133 1134 1135 1136 1137 1138 1139 1140 1141 1142 1143 1144 1145 1146 1147 1148 1149 1150 1151 1152 1153 1154 1155 1156 1157 1158 1159 1160 1161 1162 1163 1164 1165 1166 1167 1168 1169 1170 1171 1172 1173 1174 1175 1176 1177 1178 1179 1180 1181 1182 1183 1184 1185 1186 1187 1188 1189 1190 1191 1192 1193 1194 1195 1196 1197 1198 1199 1200 1201 1202 1203 1204 1205 1206 1207 1208 1209 1210 1211 1212 1213 1214 1215 1216 1217 1218 1219 1220 1221 1222 1223 1224 1225 1226 1227 1228 1229 1230 1231 1232 1233 1234 1235 1236 1237 1238 1239 1240 1241 1242 1243 1244 1245 1246 1247 1248 1249 1250 1251 1252 1253 1254 1255 1256 1257 1258 1259 1260 1261 1262 1263 1264 1265 1266 1267 1268 1269 1270 1271 1272 1273 1274 1275 1276 1277 1278 1279 1280 1281 1282 1283 1284 1285 1286 1287 1288 1289 1290 1291 1292 1293 1294 1295 1296 1297 1298 1299 1300 1301 1302 1303 1304 1305 1306 1307 1308 1309 1310 1311 1312 1313 1314 1315 1316 1317 1318 1319 1320 1321 1322 1323 1324 1325 1326 1327 1328 1329 1330 1331 1332 1333 1334 1335 1336 1337 1338 1339 1340 1341 1342 1343 1344 1345 1346 1347 1348 1349 1350 1351 1352 1353 1354 1355 1356 1357 1358 1359 1360 1361 1362 1363 1364 1365 1366 1367 1368 1369 1370 1371 1372 1373 1374 1375 1376 1377 1378 1379 1380 1381 1382 1383 1384 1385 1386 1387 1388 1389 1390 1391 1392 1393 1394 1395 1396 1397 1398 1399 1400 1401 1402 1403 1404 1405 1406 1407 1408 1409 1410 1411 1412 1413 1414 1415 1416 1417 1418 1419 1420 1421 1422 1423 1424 1425 1426 1427 1428 1429 1430 1431 1432 1433 1434 1435 1436 1437 1438 1439 1440 1441 1442 1443 1444 1445 1446 1447 1448 1449 1450 1451 1452 1453 1454 1455 1456 1457 1458 1459 1460 1461 1462 1463 1464 1465 1466 1467 1468 1469 1470 1471 1472 1473 1474 1475 1476 1477 1478 1479 1480 1481 1482 1483 1484 1485 1486 1487 1488 1489 1490 1491 1492 1493 1494 1495 1496 1497 1498 1499 1500 1501 1502 1503 1504 1505 1506 1507 1508 1509 1510 1511 1512 1513 1514 1515 1516 1517 1518 1519 1520 1521 1522 1523 1524 1525 1526 1527 1528 1529 1530 1531 1532 1533 1534 1535 1536 1537 1538 1539 1540 1541 1542 1543 1544 1545 1546 1547 1548 1549 1550 1551 1552 1553 1554 1555 1556 1557 1558 1559 1560 1561 1562 1563 1564 1565 1566 1567 1568 1569 1570 1571 1572 1573 1574 1575 1576 1577 1578 1579 1580 1581 1582 1583 1584 1585 1586 1587 1588 1589 1590 1591 1592 1593 1594 1595 1596 1597 1598 1599 1600 1601 1602 1603 1604 1605 1606 1607 1608 1609 1610 1611 1612 1613 1614 1615 1616 1617 1618 1619 1620 1621 1622 1623 1624 1625 1626 1627 1628 1629 1630 1631 1632 1633 1634 1635 1636 1637 1638 1639 1640 1641 1642 1643 1644 1645 1646 1647 1648 1649 1650 1651 1652 1653 1654 1655 1656 1657 1658 1659 1660 1661 1662 1663 1664 1665 1666 1667 1668 1669 1670 1671 1672 1673 1674 1675 1676 1677 1678 1679 1680 1681 1682 1683 1684 1685 1686 1687 1688 1689 1690 1691 1692 1693 1694 1695 1696 1697 1698 1699 1700 1701 1702 1703 1704 1